



# Notes for Sequential Circuits

---

Instructor : Pei-Yun Tsai

# Flip-Flop Inference

- Wire (port) assigned in the synchronous section

```
module FF_PN (Clock, X1, X2, Y1, Y2);
```

```
  input  Clock;
```

```
  input  X1, X2;
```

```
  output Y1, Y2;
```

```
  reg    Y1, Y2;
```


```
  always @(posedge Clock)
```

```
    Y1 <= X1;
```


```
  always @(negedge Clock)
```

```
    Y2 <= X2;
```

```
endmodule
```

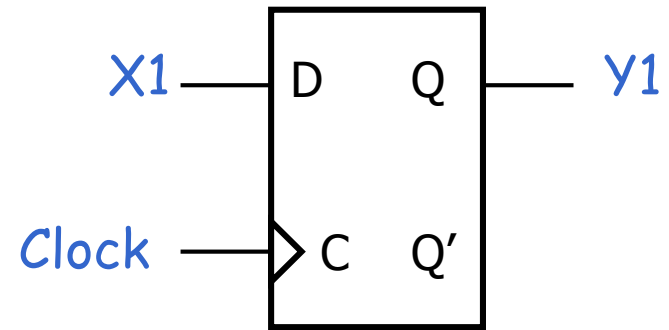

Positive-edge

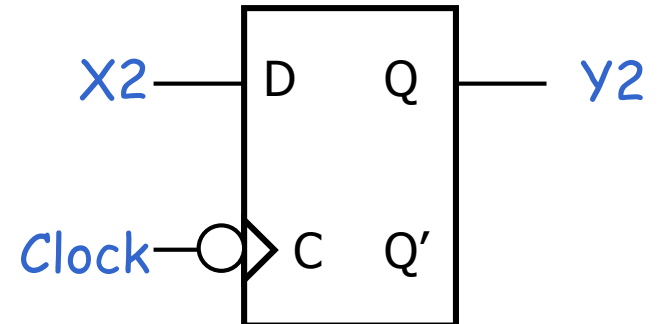

negative-edge



# Reset (1/2)

---

- Synchronous reset
  - The reset signal will only affect or reset the state of the flip-flop on the active edge of a clock.
  - Easy to synthesize
  - Problem
    - The reset could be a “late arriving signal” relative to the clock period, due to the high fanout of the reset tree.
    - The glitches occurring near the active clock edge make the flip-flop could go metastable.



## Reset (2/2)


---

- Asynchronous reset
  - Do not require a free-running clock
  - It is guaranteed not to have the reset added to the data path.
  - Problem
    - Asynchronous nature at the assertion and at the de-assertion  
If the asynchronous reset is released at or near the active clock edge of a flip-flop, the output of the flip-flop could go meta-stable and thus the reset state of the ASIC could be lost.
    - The spurious reset may be generated due to noise or glitches on the board or system reset
  - Asynchronous reset is more popular so far.

# Modeling Reset

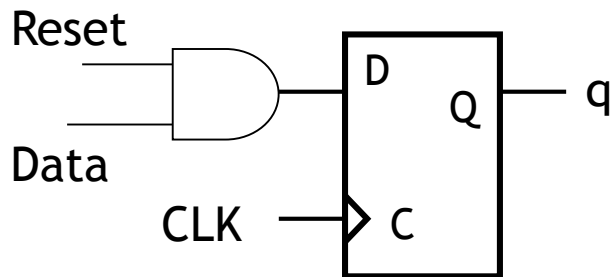
## ■ Synchronous reset

```
always@(posedge CLK)
if (!Reset) q<=1'b0;
else q<=Data;
```


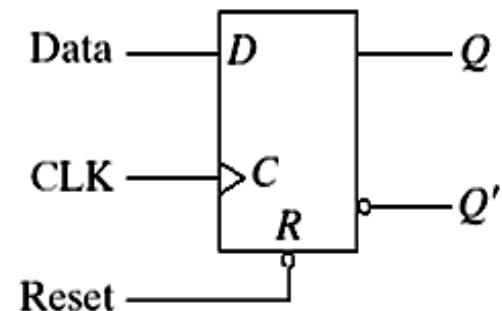
## ■ Asynchronous reset

```
always@(posedge CLK or
negedge Reset )
if (!Reset) q<=1'b0;
else q<=Data;
```





# Flip-Flop with Set/Reset

---

- Asynchronous set and reset

```
module dff3(q,d,clk,rst_n,set_n);  
output reg q,  
input d, clk, rst_n, set_n  
always @(posedge clk or negedge rst_n or negedge set_n)  
    if (!rst_n) q <= 1'b0; // asynchronous reset  
    else if (!set_n) q <= 1'b1; // asynchronous set  
    else q <= d;  
  
endmodule
```



# Flip-Flop with Load

---



- Synchronous load

```
module dff4 (q,co,d,ld,rst_n,clk);  
  output reg [7:0] q,  
  output reg co;  
  input [7:0] d;  
  input ld, rst_n, clk  
  
  always @(posedge clk or negedge rst_n)  
    if (!rst_n) {co,q} <= 9'b0; // async reset  
    else if (ld) {co,q} <= d; // sync load  
    else {co,q} <= q + 1'b1; // sync increment  
  
endmodule
```

# Timing Requirement

- Gate delay, setup time, and hold time

$t_{PLH}$	Propagation Delay from Low to High
$t_{PHL}$	Propagation Delay from High to Low
$t_{Setup}$	Setup Time
$t_{Hold}$	Hold Time

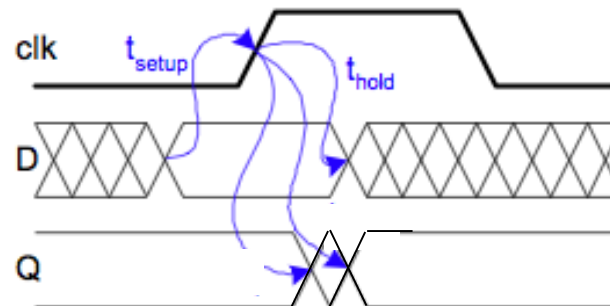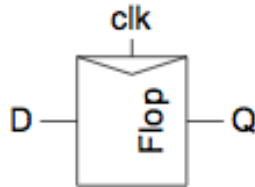

Propagation Delay






C2Q delay + gate delay (wire delay) + setup time  
= critical path delay

Maximum operating frequency =  $1/\text{critical path delay}$

# Blocking and Non-blocking Assignments

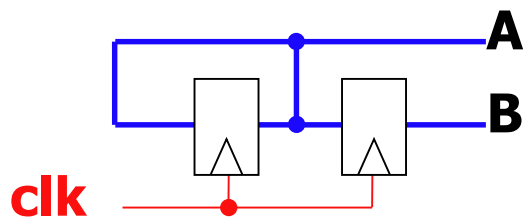
**Bad: Circuit from blocking assignment.**

```
always @(posedge clk)
begin
    b=a;
    a=b;
end
```



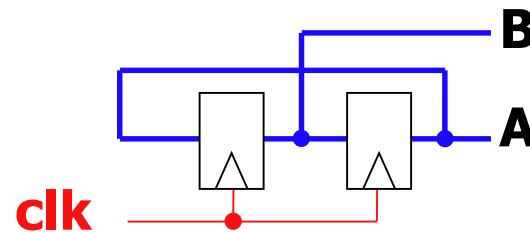**Good: Circuit from nonblocking assignment.**


```
always @(posedge clk)
begin
    b<=a;
    a<=b;
end
```





# The Simplest Shift Register

---

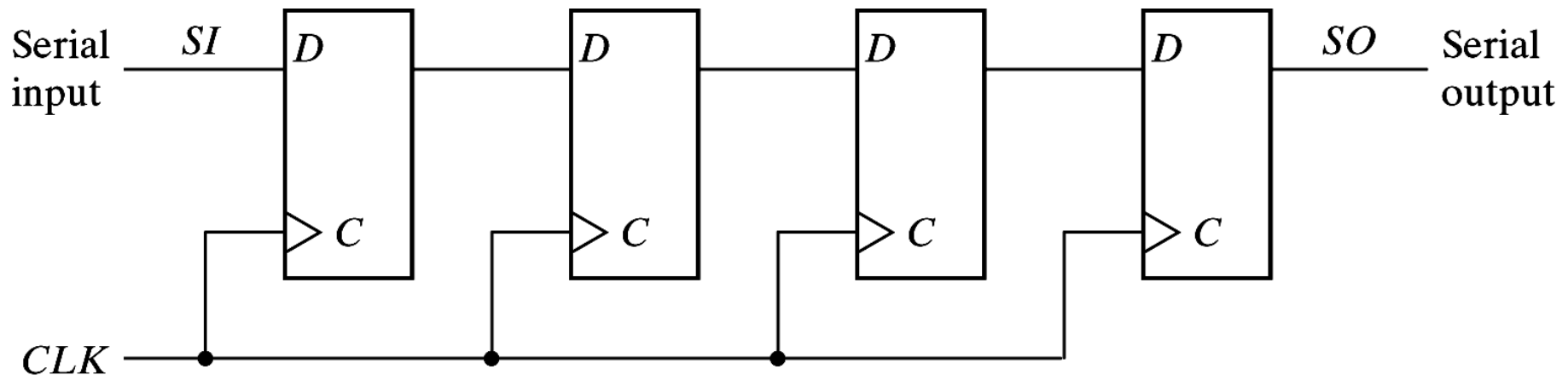



# HDL Modeling for Shift Reg.

---

## ■ Blocking assignment

```
assign SO = D;  
always @(posedge CLK) begin  
    if (reset) begin  
        A = 0; B = 0; C = 0; D = 0;  
    end  
    else begin  
        D = C;  
        C = B;  
        B = A;  
        A = SI;  
    end  
end
```

order dependent

## ■ Non-blocking assignment

```
assign SO = D;  
always @(posedge CLK) begin  
    if (reset) begin  
        A <= 0; B <= 0; C <= 0; D <= 0;  
    end  
    else begin  
        A <= SI;  
        C <= B;  
        D <= C;  
        B <= A;  
    end  
end
```

can be any order



# More Examples

---

// Blocking assignment:

initial

begin

CLR = #5 1;

CLR = #4 0;

CLR = #10 1;

end

/\* CLR is assigned 1 at time 5,  
0 at time 9, and 1 at time 19 \*/

// Non-blocking assignment:

initial

begin

CLR <= #5 1;

CLR <= #4 0;

CLR <= #10 1;

end

/\* CLR is assigned 0 at time 4,  
1 at time 5, and 1 at time 10 \*/

\* Value is undetermined if  
multiple values are assigned  
at the same time.



# Inconsistent Results

---

- The following situations may cause simulation to disagree with synthesis
  - Incomplete sensitivity list
    - Sensitivity list is ignored in synthesis routines
  - Code with delays
    - The specified delay values are also ignored
  - Non-local reference within a function
  - Order dependency of concurrent statements
  - Comparisons to X or Z
- Those cases should be avoided at all



# Parameters

---

- Parameters are used to define a constant which can be changed for each compilation.
- Common usage
  - Specify delays and widths

- `module Adder(cout, s, cin, a, b)`  
`parameter Input_Size=5;`

- `// Input port declaration`  
`input [Input_Size-1:0] a,b;`

```
Adder#(8) Myadder(.cout(C1),.s(S1),.cin(C0),.a(A1),.b(B1));
```