




# RAM and ROM

---

Instructor : Pei-Yun Tsai

# RAM Cell Array

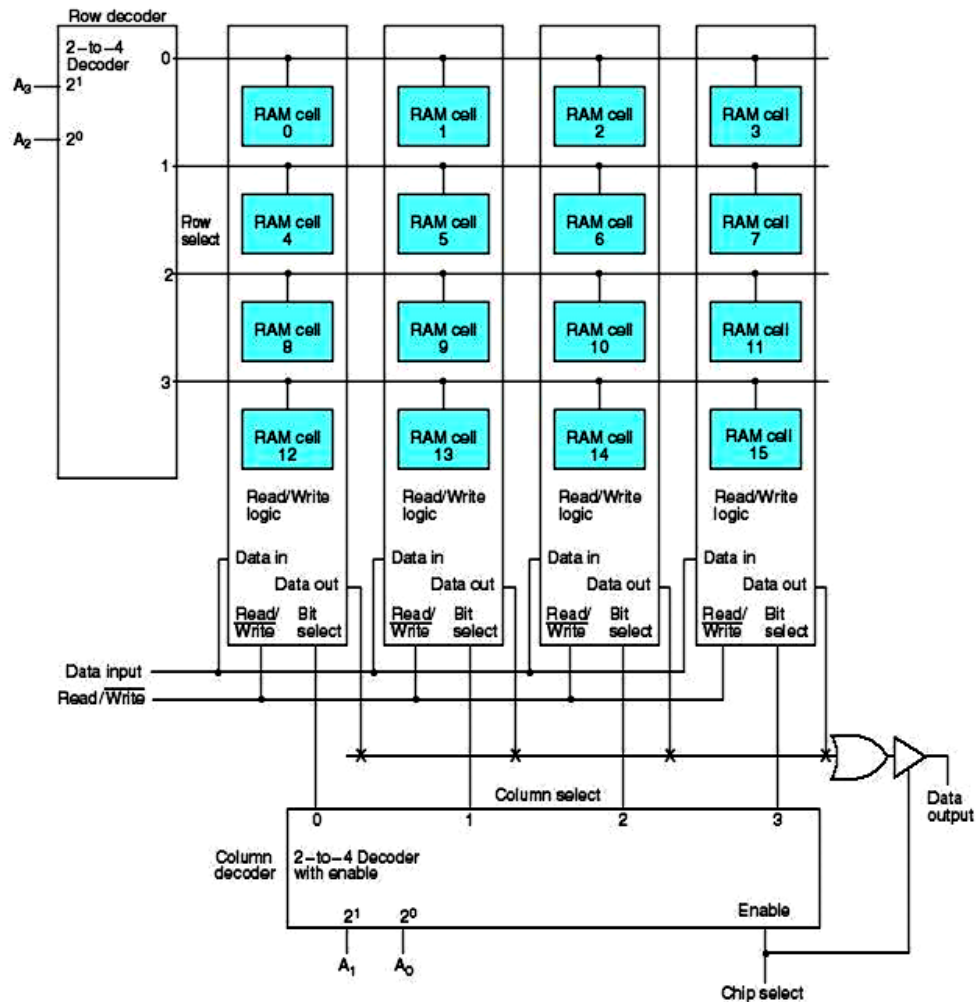



# Write and Read Operations

---

- Write to RAM

- Apply the binary address of the desired word to the **address lines**
- Apply the data bits that must be stored in memory to the **data input lines**
- Activate the **write control**


- Read from RAM

- Apply the binary address of the desired word to the **address lines**
- Activate the **read control**

 
# Coincident Decoding

- Address decoders are often divided into two parts
  - A two-dimensional scheme
- The total number of gates in decoders can be reduced


- Can arrange the memory cells to a square shape
- EX: 10-bit address  
404 = 0110010100  
X = 01100  
Y = 10100



# Timing of Synchronous Read Operation

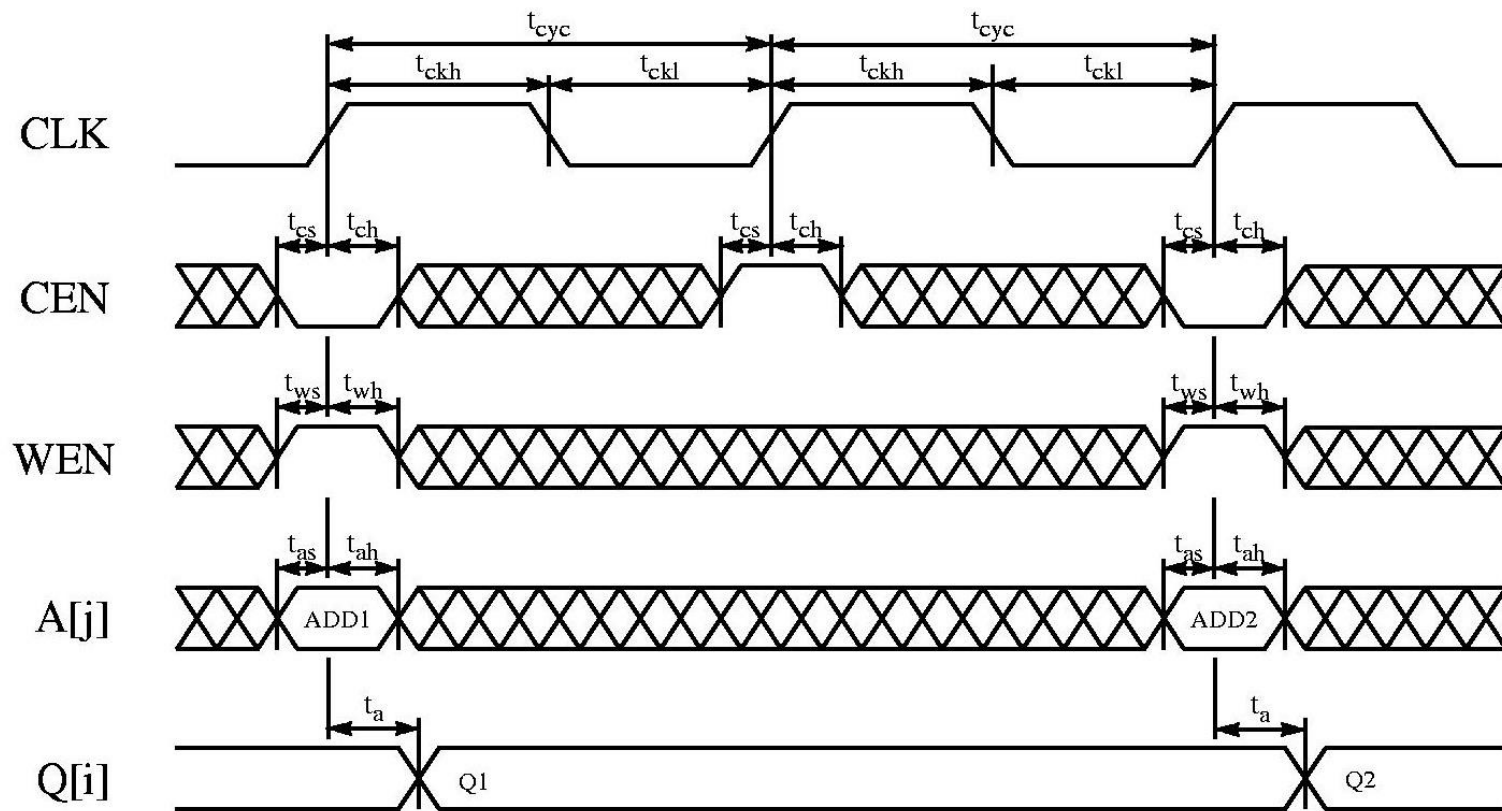

# Timing of Synchronous Write Operation

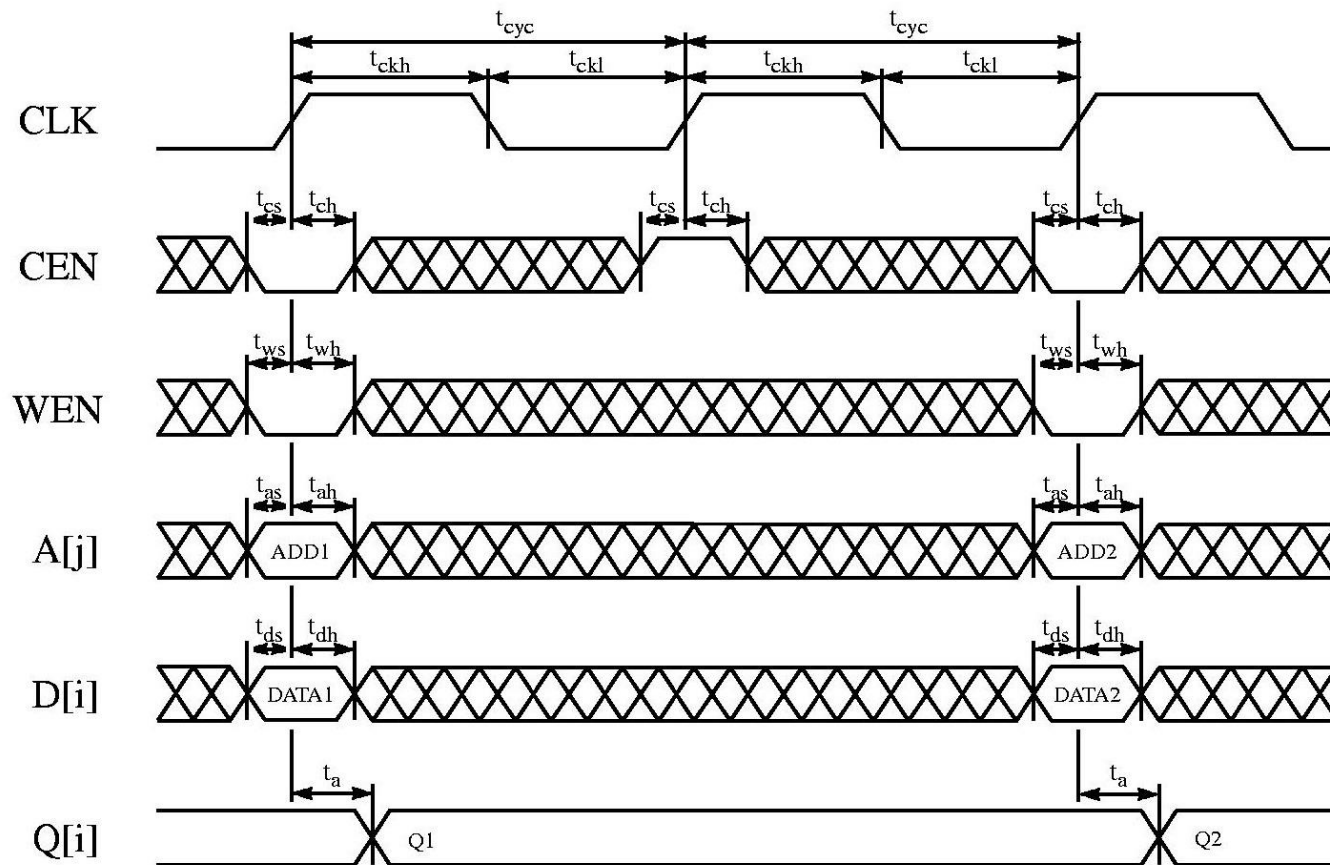



# Modeling Memory Array (1/2)

---

- The following codes do not synthesize a real SRAM module. Instead, an array of registers is constructed. If a real SRAM module is required, you need to call **SRAM compiler**.

```
reg [3:0] MemCell [7:0]; // 8 4-bit memory array
reg [3:0] RAMOut;
wire[3:0] NewData;
```

```
// Asynchronous Memory array operation
always@(MemCell[7] or NewData)
begin
    //read
    RAMOut=MemCell[7];
    //write
    MemCell[0]=NewData;
end
```



# Modeling Memory Array (2/2)

---

```
reg [3:0] MemCell [7:0]; // 8 4-bit memory array
reg [3:0] RAMOut;
wire[3:0] NewData;
```

```
// Synchronous Memory array operation
always@(posedge CLK)
begin
    //read
    RAMOut=MemCell[7];
    //write
    if (WEN)
    MemCell[0]=NewData;
end
```

Instantiation SRAM  
made by SRAM  
compiler

```
SRAM256x28
SRAMU0(.Q(dDataOut),
        .CLK(clk),
        .CEN(RAMCEN),
        .WEN(bRW),
        .A(dAdd),
        .D(dDataIn),
        .OEN(bOEN));
```





# Memory Array Initialization

- Use memory array declaration in Verilog
  - Use in testbench
  - \$readmemb, \$readmemh

```
module RAMInit;  
    reg [3:0] Memory [7:0]; // 8 4-bit memory array  
    integer i;  
    initial  
        begin  
            // read from file  
            $readmemb("init.txt", Memory);  
            for (i=0; i<8; i=i+1)  
                $display("Memory[%d]=%b",i,Memory[i]);  
        end  
endmodule
```

init.txt

```
@02  
0011 0101  
1100 1010  
  
@06  
11zz 0000
```

Result

```
Memory[0]=xxxx  
Memory[1]=xxxx  
Memory[2]=0011  
Memory[3]=0101  
Memory[4]=1100  
Memory[5]=1010  
Memory[6]=11zz  
Memory[7]=0000
```




# Read-Only Memories

---

- Read-only memories are nonvolatile
  - Retain their contents when power is removed
- Mask-programmed ROMs use one transistor per bit
  - Presence or absence determines 1 or 0

# ROM Example

- 4-word x 6-bit ROM
  - Represented with dot diagram
  - Dots indicate 1's in ROM

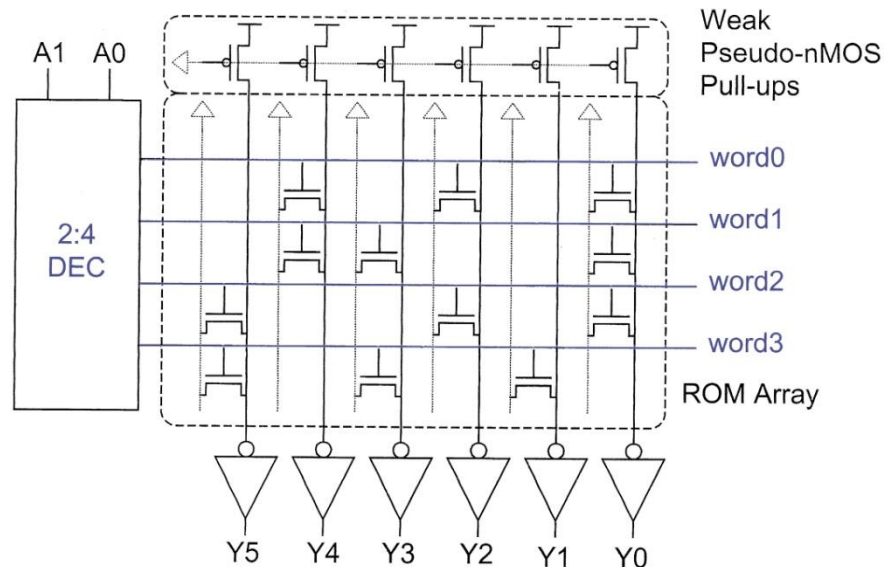


Word 0: **010101**

Word 1: **011001**

Word 2: **100101**

Word 3: **101010**

 




# Read Only Memory (1/2)

**ROM Truth Table (Partial)**

**Table 7-3**

Inputs					Outputs							
I <sub>4</sub>	I <sub>3</sub>	I <sub>2</sub>	I <sub>1</sub>	I <sub>0</sub>	A <sub>7</sub>	A <sub>6</sub>	A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		.							.			
		.							.			
		.							.			
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

# Read Only Memory (2/2)

 



# Modeling ROM (1/2)

---

```
module rom_256x8a (OE, Addr, O);
  parameter numAddr = 8;    // word depth = (2^numAddr);
  parameter numOut  = 8;    // number of Output bit width
  input             OE ; // output enable
  input [numAddr-1:0] Addr; // input address
  output [numOut-1:0] O  ; // output data
  reg [numOut-1:0] DATA; // ROM Data

  always @(Addr) begin // In this exapmle, it just use the 225 entries.
    case (Addr)         //Address      : Data
      //=====
      8'b00000000 : DATA = 8'b11111111;
      8'b00000001 : DATA = 8'b11111111;
      8'b00000010 : DATA = 8'b11111111;
      8'b00000011 : DATA = 8'b11111111;
      8'b00000100 : DATA = 8'b11111111;
      8'b00000101 : DATA = 8'b11111111;
      8'b00000110 : DATA = 8'b11111111;
      ....
```



## Modeling ROM (2/2)

---

```
8'b11011111 : DATA = 8'b01111001;
8'b11100000 : DATA = 8'b01000111;
default      : DATA = 8'bxxxxxxxx;
//=====
endcase
end
// -----
// OE low to output in Hi-Z
// OE high to output driven
// -----
assign O = (OE)? DATA : 8'bz; // not mandatory
endmodule
```

# Building Logic with ROMs

- Use ROM as lookup table containing truth table
  - $n$  inputs,  $k$  outputs requires  $2^n$  words  $\times$   $k$  bits
  - Changing function is easy - reprogram ROM
- Finite State Machine
  - $n$  inputs,  $k$  outputs,  $s$  bits of state
  - Build with  $2^{n+s} \times (k+s)$  bit ROM and  $(k+s)$  bit reg

